

CONTENTS

List of tables xv

Preface xvii

CHAPTER 1 FOUNDATIONS 1

Introduction 1

Voltage, current, and resistance 2

- 1.01 Voltage and current 2
- 1.02 The relationship between voltage and current: resistors 3
- 1.03 Voltage dividers 7
- 1.04 Voltage and current sources 7
- 1.05 Thévenin's theorem 8
- 1.06 Small signal resistance 11

Signals 13

- 1.07 Sinusoidal signals 13
- 1.08 Signal amplitudes and decibels 14
- 1.09 Other signals 14
- 1.10 Logic levels 16
- 1.11 Signal sources 17

Capacitors and ac circuits 17

- 1.12 Capacitors 18
- 1.13 *RC* Circuits: V and I versus time 20
- 1.14 Differentiators 22
- 1.15 Integrators 23

Inductors and transformers 24

- 1.16 Inductors 24
- 1.17 Transformers 24

Impedance and reactance 25

- 1.18 Frequency analysis of reactive circuits 25

1.19 *RC* Filters 29

1.20 Phasor diagrams 32

1.21 "Poles" and decibels per octave 33

1.22 Resonant circuits and active filters 33

1.23 Other capacitor applications 34

1.24 Thévenin's theorem generalized 35

Diodes and diode circuits 35

1.25 Diodes 35

1.26 Rectification 37

1.27 Power-supply filtering 37

1.28 Rectifier configurations for power supplies 38

1.29 Regulators 39

1.30 Circuit applications of diodes 40

1.31 Inductive loads and diode protection 43

Other passive components 44

1.32 Electromechanical devices 45

1.33 Indicators 47

1.34 Variable components 47

Additional exercises 48

CHAPTER 2 TRANSISTORS 50

Introduction 50

2.01 First model: current amplifier 51

Some basic transistor circuits 52

2.02 Transistor switch 52

2.03 Emitter follower 53

2.04 Emitter followers as voltage regulators 55

2.05 Emitter follower biasing 56

2.06 Transistor current source 59

2.07 Common-emitter amplifier 62

2.08 Unity-gain phase splitter 63

2.09 Transconductance 64

Ebers-Moll model applied to basic transistor circuits 65

- 2.10 Improved transistor model:
transconductance amplifier 65
- 2.11 The common-emitter amplifier
revisited 67
- 2.12 Biasing the common-emitter
amplifier 68
- 2.13 Current mirrors 71

Some amplifier building blocks 74

- 2.14 Push-pull output stages 74
- 2.15 Darlington connection 77
- 2.16 Bootstrapping 78
- 2.17 Differential amplifiers 80
- 2.18 Capacitance and Miller effect 83
- 2.19 Field-effect transistors 85

Some typical transistor circuits 85

- 2.20 Regulated power supply 85
- 2.21 Temperature controller 87
- 2.22 Simple logic with transistors and
diodes 87

Self-explanatory circuits 89

- 2.23 Bad circuits 89
- Additional exercises 89*

**CHAPTER 3
FEEDBACK AND OPERATIONAL
AMPLIFIERS 92****Introduction to feedback and operational
amplifiers 92**

- 3.01 Introduction to feedback 92
- 3.02 Operational amplifiers 93
- 3.03 The golden rules 94

Basic op-amp circuits 94

- 3.04 Inverting amplifier 94
- 3.05 Noninverting amplifier 95
- 3.06 Follower 95
- 3.07 Current sources 96
- 3.08 Basic cautions for op-amp circuits 97

An op-amp smorgasbord 98

- 3.09 Linear circuits 98
- 3.10 Nonlinear circuits 102

A detailed look at op-amp behavior 103

- 3.11 Departure from ideal op-amp
performance 103
- 3.12 Effects of op-amp limitations on circuit
behavior 107
- 3.13 Low-power and programmable
op-amps 116

**A detailed look at selected op-amp
circuits 117**

- 3.14 Logarithmic amplifier 117
- 3.15 Active peak detector 118
- 3.16 Active clamp 120
- 3.17 Absolute-value circuit 120
- 3.18 Integrators 121
- 3.19 Differentiators 122

**Op-amp operation with a single power
supply 122**

- 3.20 Biasing single-supply ac amplifiers 122
- 3.21 Single-supply op-amps 123

Comparators and Schmitt trigger 124

- 3.22 Comparators 124
- 3.23 Schmitt trigger 125

Feedback with finite-gain amplifiers 127

- 3.24 Gain equation 127
- 3.25 Effects of feedback on amplifier
circuits 127
- 3.26 Two examples of transistor amplifiers
with feedback 130

Some typical op-amp circuits 132

- 3.27 General-purpose lab amplifier 132
- 3.28 Voltage-controlled oscillator 132
- 3.29 TTL zero-crossing detector 134
- 3.30 Load-current-sensing circuit 134

Feedback amplifier frequency compensation 136

- 3.31 Gain and phase shift versus frequency 136
- 3.32 Amplifier compensation methods 137
- 3.33 Frequency response of the feedback network 139

Self-explanatory circuits 142

- 3.34 Circuit ideas 142
 - 3.35 Bad circuits 142
- Additional exercises* 142

CHAPTER 4 ACTIVE FILTERS AND OSCILLATORS 148

Active filters 148

- 4.01 Frequency response with *RC* filters 148
- 4.02 Ideal performance with *LC* filters 150
- 4.03 Enter active filters: an overview 150
- 4.04 Key filter performance criteria 152
- 4.05 Filter types 153

Active filter circuits 156

- 4.06 VCVS circuits 157
- 4.07 VCVS filter design using our simplified table 158
- 4.08 State-variable filters 160
- 4.09 Twin-T notch filters 160
- 4.10 Gyrator filter realizations 161

Oscillators 162

- 4.11 Introduction to oscillators 162
- 4.12 Relaxation oscillators 162
- 4.13 The classic timer chip: the 555 164
- 4.14 Wien bridge and *LC* oscillators 165
- 4.15 *LC* oscillators 166
- 4.16 Quartz-crystal oscillators 167

Self-explanatory circuits 171

- 4.17 Circuit ideas 171
- Additional exercises* 171

CHAPTER 5 VOLTAGE REGULATORS AND POWER CIRCUITS 172

Basic regulator circuits with the classic 723 172

- 5.01 The 723 regulator 172
- 5.02 Positive regulator 174
- 5.03 High-current regulator 176

Heat and power design 177

- 5.04 Power transistors and heat sinking 177
- 5.05 Foldback current limiting 180
- 5.06 Overvoltage crowbars 182
- 5.07 Further considerations in high-current power-supply design 183
- 5.08 Programmable supplies 185
- 5.09 Power-supply circuit example 185

The unregulated supply 187

- 5.10 ac Line components 187
- 5.11 Transformer 189
- 5.12 dc Components 190

Voltage references 192

- 5.13 Zener diodes 192
- 5.14 Bandgap (V_{BE}) reference 195

Three-terminal and four-terminal regulators 199

- 5.15 Three-terminal regulators 199
- 5.16 Four-terminal regulators 199
- 5.17 Three-terminal adjustable regulators 202
- 5.18 Additional comments about 3-terminal regulators 202

Special-purpose power-supply circuits 204

- 5.19 Dual-tracking regulators 204
- 5.20 High-voltage regulators 207
- 5.21 Switching regulators 210
- 5.22 dc-to-dc Converters 211
- 5.23 Energy-storage inductor 213
- 5.24 Constant-current supplies 216

Self-explanatory circuits 218

- 5.25 Circuit ideas 218
- 5.26 Bad circuits 218
- Additional exercises 218*

**CHAPTER 6
FIELD-EFFECT TRANSISTORS 223**

FET characteristics 223

- 6.01 JFETs 223
- 6.02 MOSFETs 224
- 6.03 Universal FET characteristics 225
- 6.04 FET drain characteristics 226
- 6.05 Manufacturing spread of FET characteristics 229

Basic FET circuits 231

- 6.06 JFET current sources 231
- 6.07 FET amplifiers 232
- 6.08 Source followers 234
- 6.09 JFET input impedance and gate leakage 237
- 6.10 FETs as variable resistors 240
- 6.11 Op-amp controlled current sources 241

FET switches 242

- 6.12 FET linear switches 242
- 6.13 FETs as logic switches 244
- 6.14 FET linear switch applications 245
- 6.15 Limitations of FET switches 247

Some additional FET circuit ideas 250

- 6.16 Amplifiers 250
- 6.17 Pinch-off reference 253
- 6.18 Switch circuits 253
- 6.19 BiFET integrated circuits 255
- 6.20 Power MOSFETs 256

Self-explanatory circuits 257

- 6.21 Circuit ideas 257
- 6.22 Bad circuits 257

**CHAPTER 7
PRECISION CIRCUITS AND LOW-
NOISE TECHNIQUES 262**

Precision op-amp design techniques 262

- 7.01 Precision versus dynamic range 262
- 7.02 Error budget 263
- 7.03 Example circuit: precision amplifier with automatic null offset 263
- 7.04 A precision-design error budget 264
- 7.05 Component errors 264
- 7.06 Amplifier input errors 266
- 7.07 Amplifier output errors 271

**Differential and instrumentation
amplifiers 279**

- 7.08 Differencing amplifier 279
- 7.09 Standard three-op-amp instrumentation amplifier 282

Amplifier noise 286

- 7.10 Origins and kinds of noise 288
- 7.11 Signal-to-noise ratio and noise figure 290
- 7.12 Transistor amplifier voltage and current noise 291
- 7.13 Low-noise design with transistors 293
- 7.14 FET noise 298
- 7.15 Selecting low-noise transistors 299
- 7.16 Noise in differential and feedback amplifiers 299

**Noise measurements and noise
sources 303**

- 7.17 Measurement without a noise source 303
- 7.18 Measurement with noise source 304
- 7.19 Noise and signal sources 305
- 7.20 Bandwidth limiting and rms voltage measurement 306

Interference: shielding and grounding 307

- 7.21 Interference 307
- 7.22 Signal grounds 308
- 7.23 Grounding between instruments 309

Self-explanatory circuits 313

- 7.24 Circuit ideas 313
- Additional exercises* 313

CHAPTER 8 DIGITAL ELECTRONICS 316

Basic logic concepts 316

- 8.01 Digital versus analog 316
- 8.02 Logic states 317
- 8.03 Number codes 318
- 8.04 Gates and truth tables 321
- 8.05 Discrete circuits for gates 323
- 8.06 Gate circuit example 324
- 8.07 Assertion-level logic notation 325

TTL and CMOS 326

- 8.08 Catalog of common gates 326
- 8.09 IC gate circuits 328
- 8.10 TTL and CMOS characteristics 328
- 8.11 Three-state and open-collector devices 329

Combinational logic 331

- 8.12 Logic identities 332
- 8.13 Minimization and Karnaugh maps 333
- 8.14 Combinational functions available as ICs 334
- 8.15 Implementing arbitrary truth tables 338

Sequential logic 341

- 8.16 Devices with memory: flip flops 341
- 8.17 Clocked flip-flops 343
- 8.18 Combining memory and gates: sequential logic 347
- 8.19 Synchronizer 349

Monostable multivibrators 351

- 8.20 One-shot characteristics 351
- 8.21 Monostable circuit example 353
- 8.22 Cautionary notes about monostables 354
- 8.23 Timing with counters 356

Sequential functions available as ICs 357

- 8.24 Latches and registers 357
- 8.25 Counters 358
- 8.26 Shift registers 359
- 8.27 Miscellaneous sequential functions 362

Some typical digital circuits 365

- 8.28 Modulo- n counter 365
- 8.29 Multiplexed LED digital display 365
- 8.30 Siderial telescope drive 367
- 8.31 FIFO-buffered keyboard 370
- 8.32 n -Pulse generator 371

Logic pathology 373

- 8.33 dc Problems 374
- 8.34 Switching problems 374
- 8.35 Congenital weaknesses of TTL and CMOS 375

Self-explanatory circuits 377

- 8.36 Circuit ideas 377
- 8.37 Bad circuits 377
- Additional exercises* 377

CHAPTER 9 DIGITAL MEETS ANALOG 380

TTL and CMOS logic interfacing 380

- 9.01 TTL and CMOS logic families 380
- 9.02 Input and output characteristics of TTL and CMOS 382
- 9.03 Interfacing between TTL and CMOS 384
- 9.04 Driving TTL and CMOS inputs 386
- 9.05 Driving digital logic from comparators and op-amps 388
- 9.06 Some comments about logic inputs 389
- 9.07 Comparators 390
- 9.08 Driving external digital loads from TTL and CMOS 393

n -channel and p -channel MOS LSI interfacing 398

- 9.09 NMOS inputs 398
- 9.10 NMOS outputs 399
- 9.11 PMOS inputs 400

- 9.12 PMOS outputs 401
- 9.13 Summarizing MOS family characteristics 402

Digital signals and long wires 402

- 9.14 On-board interconnections 403
- 9.15 Inter-card connections 405
- 9.16 Data buses 405
- 9.17 Driving cables 406

Analog/digital conversion 408

- 9.18 Introduction to A/D conversion 408
- 9.19 Digital-to-analog-converters (DACs) 410
- 9.20 Time domain (averaging) DACs 413
- 9.21 Multiplying DACs 414
- 9.22 Analog-to-digital converters 415
- 9.23 Charge-balancing techniques 417

Some A/D conversion examples 420

- 9.24 16-Channel A/D data acquisition system 420
- 9.25 $3\frac{1}{2}$ -Digit voltmeter 423
- 9.26 Delta-sigma continuous-integrating converter 423
- 9.27 Coulomb meter 425

Phase-locked loops 428

- 9.28 Introduction to phase-locked loops 428
- 9.29 PLL components 429
- 9.30 PLL design 431
- 9.31 Design example: frequency multiplier 432
- 9.32 PLL capture and lock 435
- 9.33 Some PLL applications 436

Pseudo-random-bit sequences and noise generation 437

- 9.34 Digital noise generation 437
- 9.35 Feedback shift register sequences 438
- 9.36 Analog noise generation from maximal-length sequences 440
- 9.37 Power spectrum of shift register sequences 440
- 9.38 Low-pass filtering 442
- 9.39 Wrap-up 443
- 9.40 Digital filters 446

Self-explanatory circuits 448

- 9.41 Circuit ideas 448
- 9.42 Bad circuits 451
- Additional exercises* 451

CHAPTER 10 MINICOMPUTERS 453

Minicomputers, microcomputers, and microprocessors 453

- 10.01 Computer architecture 454

A computer instruction set 456

- 10.02 Assembly language and machine language 456
- 10.03 The MC-16 instruction set 457
- 10.04 A programming example 458

Bus signals and interfacing 458

- 10.05 Fundamental bus signals: data, address, strobe 459
- 10.06 Programmed I/O: data out 459
- 10.07 Programmed I/O: data in 461
- 10.08 Programmed I/O: status registers 462
- 10.09 Interrupts 465
- 10.10 Interrupt handling method I: device polling 466
- 10.11 Interrupt handling method II: vectored interrupt 466
- 10.12 Direct memory access 468
- 10.13 Synchronous versus asynchronous communication 469
- 10.14 Connecting peripherals to the computer 470

Software system concepts 472

- 10.15 Programming 472
- 10.16 Operating systems, files, and use of memory 473

Data communications concepts 475

- 10.17 Alphanumeric codes and serial communication 475
- 10.18 Numeric data interfacing 478
- Additional exercises* 481

CHAPTER 11 MICROPROCESSORS 484

A detailed look at the 8085 485

- 11.1 Architecture 485
- 11.2 Internal operation 487
- 11.3 Instruction set 489
- 11.4 Machine-language representation 495

A complete design example: 6-channel event counter 501

- 11.5 Circuit design 501
- 11.6 Programming the 6-channel event counter 505
- 11.7 Program timing and performance 512

Microprocessor support chips 514

- 11.8 Medium-scale integration 514
- 11.9 Peripheral LSI chips 517
- 11.10 Memory 521
- 11.11 Designing a system with LSI 523

Further topics in microprocessor system design 529

- 11.12 The S100 bus 529
- 11.13 Other microprocessors 530
- 11.14 Evaluation boards, development systems, and emulators 532

CHAPTER 12 ELECTRONIC CONSTRUCTION TECHNIQUES 536

Prototyping methods 536

- 12.01 Breadboards 536
- 12.02 PC prototyping boards 537
- 12.03 Wire-wrap panels 538

Printed circuits 540

- 12.04 PC board fabrication 540
- 12.05 PC board design 542
- 12.06 Stuffing PC boards 544
- 12.07 Some further thoughts on PC boards 546

Instrument construction 546

- 12.08 Housing circuit boards in an instrument 546
- 12.09 Cabinets 547
- 12.10 Construction hints 548
- 12.11 Cooling 549
- 12.12 Some electrical hints 550
- 12.13 Where to get components 553

CHAPTER 13 HIGH-FREQUENCY AND HIGH-SPEED TECHNIQUES 554

High-frequency amplifiers 554

- 13.01 Transistor amplifiers at high frequencies: first look 554
- 13.02 High-frequency amplifiers: the ac model 555
- 13.03 A high-frequency calculation example 557
- 13.04 High-frequency amplifier configurations 558
- 13.05 A wideband design example 560
- 13.06 Some refinements to the ac model 562
- 13.07 The shunt-series pair 562
- 13.08 Modular amplifiers 564

Radiofrequency circuit elements 565

- 13.09 Transmission lines 565
- 13.10 Stubs, baluns, and transformers 567
- 13.11 Tuned amplifiers 568
- 13.12 Radiofrequency circuit elements 570

Radiofrequency communications: AM 573

- 13.13 Some communications concepts 573
- 13.14 Amplitude modulation 573
- 13.15 Superheterodyne receiver 575

Advanced modulation methods 576

- 13.16 Single sideband 576
- 13.17 Frequency modulation 577
- 13.18 Frequency-shift keying 579
- 13.19 Pulse-modulation schemes 579

Radiofrequency circuit tricks 580

- 13.20 Special construction techniques 580
- 13.21 Exotic RF amplifiers and devices 581

High-speed switching 582

13.22 Transistor model and equations 582

Some switching-speed examples 585

13.23 High-voltage driver 585
 13.24 Open-collector bus driver 586
 13.25 Example: photomultiplier preamp 587
 13.26 Circuit ideas 589
Additional exercises 589

**CHAPTER 14
 MEASUREMENTS AND SIGNAL
 PROCESSING 591**

Overview 591

Measurement transducers 592

14.01 Temperature 592
 14.02 Light level 597
 14.03 Strain and displacement 601
 14.04 Acceleration, pressure, force,
 velocity 605
 14.05 Magnetic field 607
 14.06 Vacuum gauges 608
 14.07 Particle detectors 608
 14.08 Biological and chemical voltage
 probes 612

**Precision standards and precision
 measurements 615**

14.09 Frequency standards 615
 14.10 Frequency, period, and time-interval
 measurements 617
 14.11 Voltage and resistance standards and
 measurements 623

Bandwidth-narrowing techniques 624

14.12 The problem of signal-to-noise
 ratio 624
 14.13 Signal averaging and multichannel
 averaging 624
 14.14 Making a signal periodic 627
 14.15 Lock-in detection 628
 14.16 Pulse height analysis 631
 14.17 Time-to-amplitude converters 632

**Spectrum analysis and Fourier
 transforms 633**

14.18 Spectrum analyzers 633
 14.19 Off-line spectrum analysis 635

APPENDIXES

**Appendix A
 The oscilloscope 638**

**Appendix B
 Math review 642**

**Appendix C
 The 5% resistor color code 645**

**Appendix D
 1% Precision resistors 646**

**Appendix E
 How to draw schematic diagrams 647**

**Appendix F
 Load lines 650**

**Appendix G
 Transistor saturation 652**

**Appendix H
 LC Butterworth filters 654**

**Appendix I
 Electronics magazines and journals 657**

**Appendix J
 IC generic types 659**

**Appendix K
 Data sheets 661**
 1N914 signal diode 662
 2N4400-1 NPN transistor 666
 LM394 NPN matched pair 671
 LF355-7 JFET operational amplifier 677
 LM317 3-terminal adjustable regulator 691
 96LS02 TTL monostable multivibrator 699

Bibliography 705

Index 709